

# Digital Logic & Digital Systems

4004CEM

Computer Architecture & Networks

# Introduction to Logic Circuit Design

- Truth tables
- Boolean expressions
- Symbols of logic operators
- Basic logic gates
- Proof using truth tables
- Logic circuits and transmission formulae, equivalent circuits
- Standard results
- NAND and NOR gates
- XOR and XNOR gates

**BITS: Logic 1 or Logic 0 (+5volts or 0volts)**

**Use Logic Circuits** to store/manipulate them.

**Boolean expressions** to design and describe the circuits.

**Example:** Derive the logical expression for the output P so that P is 1 (true) if any one of the inputs A,B,C is true or all of the inputs are true.

### **Truth Table**

required or actual output down the RHS for **every possible input combination**

<b>A</b>	<b>B</b>	<b>C</b>	<b>P</b>	
<b>0</b>	<b>0</b>	<b>0</b>	<b>0</b>	
<b>0</b>	<b>0</b>	<b>1</b>	<b>1</b>	*
<b>0</b>	<b>1</b>	<b>0</b>	<b>1</b>	*
<b>0</b>	<b>1</b>	<b>1</b>	<b>0</b>	
<b>1</b>	<b>0</b>	<b>0</b>	<b>1</b>	*
<b>1</b>	<b>0</b>	<b>1</b>	<b>0</b>	
<b>1</b>	<b>1</b>	<b>0</b>	<b>0</b>	
<b>1</b>	<b>1</b>	<b>1</b>	<b>1</b>	*


## Boolean Expressions

**P = 1      if    A=0 AND B=0 AND C=1  
                 OR A=0 AND B=1 AND C=0  
                 OR A=1 AND B=0 AND C=0  
                 OR A=1 AND B=1 AND C=1**

If the variable value is 0 the variable is written with a **bar** over it or with an **exclamation mark** before it.


$$\mathbf{P = \overline{A}.\overline{B}.C + \overline{A}.B.\overline{C} + A.\overline{B}.\overline{C} + A.B.C}$$

## Basic Gates

 


OR

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

 

AND

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

 

NOT

A	X
0	1
1	0

A I

**For OR:** the output is high if **either A OR B** is high


**For AND:** the output is high only if **A AND B** is high

A B  
I I

**For NOT:** the output is **the inverse** of the input i.e. it is **NOT** the input

I > 0  
0 > I

## The Inverter

 


The inverter performs the Boolean **NOT** operation. When the input is LOW, the output is HIGH; when the input is HIGH, the output is LOW.

Input	Output
$A$	$X$
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)


The **NOT** operation (complement) is shown with an overbar. Thus, the Boolean expression for an inverter is  $X = \overline{A}$ .




## The Inverter

 



Example waveforms:

 

 A group of inverters can be used to form the 1's complement of a binary number:



## The AND Gate

 
 


The **AND** gate produces a HIGH output when all inputs are HIGH; otherwise, the output is LOW. For a 2-input gate, the truth table is


Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1

The **AND** operation is usually shown with a dot between the variables but it may be implied (no dot). Thus, the AND operation is written as  $X = A \cdot B$  or  $X = AB$ .

## The AND Gate

  

Example waveforms:

 



The AND operation is used in computer programming as a selective mask. If you want to retain certain bits of a binary number but reset the other bits to 0, you could set a mask with 1's in the position of the retained bits.

## Example

If the binary number 10100011 is ANDed with the mask 00001111, what is the result?

00000011

## The OR Gate

 
 


The **OR gate** produces a HIGH output if any input is HIGH; if all inputs are LOW, the output is LOW. For a 2-input gate, the truth table is


Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

The **OR** operation is shown with a plus sign (+) between the variables. Thus, the OR operation is written as  $X = A + B$ .

## The OR Gate

  

Example waveforms:

 

The OR operation can be used in computer programming to set certain bits of a binary number to 1.


### Example

ASCII letters have a 1 in the bit 5 position for lower case letters and a 0 in this position for capitals. (Bit positions are numbered from right to left starting with 0.) What will be the result if you OR an ASCII letter with the 8-bit mask 00100000?

### Solution

The resulting letter will be lower case.


## Proof Using Truth Tables

 

A	B	C	G1	G2	G3	G4
0	0	0			1	1
0	0	1	1	1	1	1
0	1	0	1	0	0	0
0	1	1	1	0	0	0
1	0	0	0	1	0	0
1	0	1	0	1	0	0
1	1	0	0	0	0	0
1	1	1	0	0	0	0

## Drawing Logic Circuits from Transmission Formulae

$$X = A.(B + C) + D.E$$

 

## Equivalent Circuits

Complicated logic circuits can often be reduced to much simpler 'equivalent' circuits

Truth tables can be used to test equivalence

$$X = A + B.C \quad \text{and} \quad Y = (A + B).(A + C)$$

A	B	C	BC	X	A+B	A+C	Y
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

we are able to conclude that:

$$A + B.C = (A + B).(A + C)$$



## Standard Boolean Algebra rules:

### Commutative Laws

$$A.B = B.A$$

$$A+B = B+A$$

### Associative Laws

$$A.(B.C) = (A.B).C$$

$$A+(B+C) = (A+B)+C$$

### Distributive law

$$A(B + C) = A.B + A.C$$

**some simple obvious(!) results:**

$$\mathbf{A.A = A}$$

$$\mathbf{A + A = A}$$

$$\mathbf{A.\overline{A} = 0}$$

$$\mathbf{A + \overline{A} = 1}$$

$$\mathbf{A.1 = A}$$

$$\mathbf{A + 1 = 1}$$

$$\mathbf{A.0 = 0}$$

$$\mathbf{A + 0 = A}$$

$$\mathbf{\overline{\overline{A}} = A}$$

## DeMorgan's Laws

Two further (less obvious!) results:

$$\overline{(A + B)} = \overline{A} \cdot \overline{B}$$

and

$$\overline{(A \cdot B)} = \overline{A} + \overline{B}$$

Note how the application of the inverse operator changes AND to OR and vice versa.

Quick method: to change an OR to an AND or vice versa, i) break the line ii) change the sign.

## **Simplifying Circuits**

**Example 1: To show that  $(A + B)(A + C) = A + B.C$**

## Simplifying Circuits

**Example 1: To show that  $(A + B)(A + C) = A + B.C$**

$$(A + B)(A + C) = A.A + A.C + B.A + B.C$$

$$A.A + A.C + B.A + B.C = A.1 + A.C + B.A + B.C$$

$$A.1 + A.C + B.A + B.C = A.(1 + C + B) + B.C$$

$$A.(1 + C + B) + B.C = A.1 + B.C$$

$$(A + B)(A + C) = A + B.C$$

**Example 2:** To simplify  $XY + X\bar{Y}$

**Example 2:** To simplify  $XY + X\bar{Y}$

$$XY + X\bar{Y} = X.(Y + \bar{Y})$$

$$XY + X\bar{Y} = X.(Y + \bar{Y}) = X.1$$

$$XY + X\bar{Y} = X.1 = X$$

**Example 3:**

**To simplify the expression  $(A + B).(A + C).(A + D)$**

**From example 1  $(A + B).(A + C) = (A + B.C)$**

$$(A + B).(A + C).(A + D) = (A + B.C).(A + D)$$

$$(A + B.C).(A + D) = A.A + A.D + B.C.A + B.C.D$$



$$(A + B.C).(A + D) = A.(1 + D + B.C) + B.C.D$$

$$(A + B.C).(A + D) = A.1 + B.C.D$$

$$\text{So } (A + B)(A + C)(A + D) = A + B.C.D$$



## The NAND Gate

  


The **NAND** gate produces a LOW output when all inputs are HIGH; otherwise, the output is HIGH. For a 2-input gate, the truth table is



Inputs		Output
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

The **NAND** operation is shown with a dot between the variables and an overbar covering them. Thus, the NAND operation is written as  $X = \overline{A \cdot B}$  (Alternatively,  $X = \overline{AB}$ .)


# The NAND Gate

 



2-input "AND" gate plus a "NOT" gate

  

Example waveforms:

 

## The NOR Gate

 
 


The **NOR gate** produces a LOW output if any input is HIGH; if all inputs are HIGH, the output is LOW. For a 2-input gate, the truth table is


Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	0

The **NOR** operation is shown with a plus sign (+) between the variables and an overbar covering them. Thus, the NOR operation is written as  $X = \overline{A + B}$ .

## The NOR Gate

  

Example waveforms:


 


The NOR operation will produce a LOW if any input is HIGH.


**Example** When is the LED is ON for the circuit shown?

**Solution**

## The NOR Gate

  

Example waveforms:

 


The NOR operation will produce a LOW if any input is HIGH.

**Example**


When is the LED is ON for the circuit shown?

 **Solution**

The LED will be on when none of the four inputs are HIGH.



## The XOR function

 

**XOR**



$$A \oplus B = A.\bar{B} + \bar{A}.B$$

The truth table:

**XOR**


A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

## The XOR Gate

  

The **XOR** gate produces a HIGH output only when both inputs are at opposite logic levels. The truth table is



Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

 


The **XOR** operation is written as  $X = \bar{A}B + A\bar{B}$ .

Alternatively, it can be written with a circled plus sign between the variables as  $X = A \oplus B$ .

## The XOR Gate

  

Example waveforms:

 



Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.

## Question


If the *A* and *B* waveforms are both inverted for the above waveforms, how is the output affected?



## The XOR Gate

  

Example waveforms:

 


Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.

## Question

If the *A* and *B* waveforms are both inverted for the above waveforms, how is the output affected?

There is no change in the output.
 
## The inverse of the XOR function (XNOR)



**XNOR**



<b>A</b>	<b>B</b>	<b>X</b>
0	0	1
0	1	0
1	0	0
1	1	1

$$\overline{A} . \overline{B} + A . B$$

From the above truth table:

$$\overline{(A \oplus B)} = \overline{A} . \overline{B} + A . B$$

## The XNOR Gate

 
 


The **XNOR** gate produces a HIGH output only when both inputs are at the same logic level. The truth table is


Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

The **XNOR** operation shown as  $X = \bar{A}\bar{B} + AB$ . Alternatively, the XNOR operation can be shown with a circled dot between the variables. Thus, it can be shown as  $X = A \odot B$ .

## The XNOR Gate

  

Example waveforms:


 


Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.


### Question

If the *A* waveform is inverted but *B* remains the same, how is the output affected?

## The XNOR Gate

  

Example waveforms:

 

Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.

### Question

If the *A* waveform is inverted but *B* remains the same, how is the output affected?

The output will be inverted.

END